



Design with Operational Amplifiers and Analog Integrated Circuits – 3rd Edition

Sergio Franco - McGraw-Hill, 2002 - ISBN 0-07-232084-2

Contents

Preface

| | |
|---|-----|
| 1 Operational Amplifier Fundamentals | 1 |
| 1.1 Amplifier Fundamentals | 2 |
| 1.2 The Operational Amplifier | 5 |
| 1.3 Basic Op Amp Configurations | 8 |
| 1.4 Ideal Op Amp Circuit Analysis | 15 |
| 1.5 Negative Feedback | 23 |
| 1.6 Feedback in Op Amp Circuits | 29 |
| 1.7 The Loop Gain | 37 |
| 1.8 Op Amp Powering | 41 |
| Problems | 47 |
| Bibliography | 58 |
| Appendix 1A Standard Resistor Values | 58 |
| 2 Circuits with Resistive Feedback | 60 |
| 2.1 Current-to-Voltage Converters | 61 |
| 2.2 Voltage-to-Current Converters | 63 |
| 2.3 Current Amplifiers | 71 |
| 2.4 Difference Amplifiers | 73 |
| 2.5 Instrumentation Amplifiers | 79 |
| 2.6 Instrumentation Applications | 86 |
| 2.7 Transducer Bridge Amplifiers | 91 |
| Problems | 98 |
| References | 105 |
| 3 Active Filters: Part I | 106 |
| 3.1 The Transfer Function | 109 |
| 3.2 First-Order Active Filters | 115 |
| 3.3 Audio Filter Applications | 121 |
| 3.4 Standard Second-Order Responses | 126 |
| 3.5 KRC Filters | 133 |
| 3.6 Multiple-Feedback Filters | 141 |
| 3.7 State-Variable and Biquad Filters | 144 |
| 3.8 Sensitivity | 150 |
| Problems | 153 |
| References | 158 |
| 4 Active Filters: Part II | 160 |
| 4.1 Filter Approximations | 161 |
| 4.2 Cascade Design | 166 |
| 4.3 Generalized Impedance Converters | 175 |
| 4.4 Direct Design | 181 |
| 4.5 The Switched Capacitor | 187 |
| 4.6 Switched-Capacitor Filters | 192 |

| | |
|--|-----|
| 4.7 Universal SC Filters | 198 |
| Problems | 204 |
| References | 210 |
| 5 Static Op Amp Limitations | 211 |
| 5.1 Simplified Op Amp Circuit Diagram | 212 |
| 5.2 Input Bias and Offset Currents | 217 |
| 5.3 Low-Input-Bias-Current Op Amps | 221 |
| 5.4 Input Offset Voltage | 225 |
| 5.5 Low-Input-Offset-Voltage Op Amps | 230 |
| 5.6 Input Offset-Error Compensation | 235 |
| 5.7 Maximum Ratings | 240 |
| Problems | 244 |
| References | 248 |
| Appendix 5A Data Sheets of the μ A741 Op Amp | 249 |
| 6 Dynamic Op Amp Limitations | 258 |
| 6.1 Open-Loop Response | 259 |
| 6.2 Closed-Loop Response | 263 |
| 6.3 Input and Output Impedances | 269 |
| 6.4 Transient Response | 275 |
| 6.5 Effect of Finite GBP on Integrator Circuits | 283 |
| 6.6 Effect of Finite GBP on Filters | 289 |
| 6.7 Current-Feedback Amplifiers | 293 |
| Problems | 303 |
| References | 309 |
| 7 Noise | 311 |
| 7.1 Noise Properties | 313 |
| 7.2 Noise Dynamics | 317 |
| 7.3 Sources of Noise | 322 |
| 7.4 Op Amp Noise | 328 |
| 7.5 Noise in Photodiode Amplifiers | 335 |
| 7.6 Low-Noise Op Amps | 339 |
| Problems | 342 |
| References | 346 |
| 8 Stability | 347 |
| 8.1 The Stability Problem | 348 |
| 8.2 Stability in Constant-GBP Op Amp Circuits | 356 |
| 8.3 Internal Frequency Compensation | 365 |
| 8.4 External Frequency Compensation | 374 |
| 8.5 Stability in CFA Circuits | 381 |
| 8.6 Composite Amplifiers | 384 |
| Problems | 390 |
| References | 396 |
| 9 Nonlinear Circuits | 398 |
| 9.1 Voltage Comparators | 399 |
| 9.2 Comparator Applications | 407 |
| 9.3 Schmitt Triggers | 416 |
| 9.4 Precision Rectifiers | 422 |
| 9.5 Analog Switches | 428 |
| 9.6 Peak Detectors | 433 |
| 9.7 Sample-and-Hold Amplifiers | 437 |
| Problems | 443 |
| References | 448 |

| | |
|---|-----|
| 10 Signal Generators | 449 |
| 10.1 Sine Wave Generators | 451 |
| 10.2 Multivibrators | 457 |
| 10.3 Monolithic Timers | 465 |
| 10.4 Triangular Wave Generators | 471 |
| 10.5 Sawtooth Wave Generators | 476 |
| 10.6 Monolithic Waveform Generators | 478 |
| 10.7 <i>V-F</i> and <i>F-V</i> Converters | 486 |
| Problems | 492 |
| References | 497 |
| | |
| 11 Voltage References and Regulators | 499 |
| 11.1 Performance Specifications | 500 |
| 11.2 Voltage References | 506 |
| 11.3 Voltage-Reference Applications | 512 |
| 11.4 Linear Regulators | 519 |
| 11.5 Linear-Regulator Applications | 527 |
| 11.6 Switching Regulators | 535 |
| 11.7 Monolithic Switching Regulators | 544 |
| Problems | 551 |
| References | 557 |
| | |
| 12 D-A and A-D Converters | 559 |
| 12.1 Performance Specifications | 561 |
| 12.2 D-A Conversion Techniques | 567 |
| 12.3 Multiplying DAC Applications | 580 |
| 12.4 A-D Conversion Techniques | 584 |
| 12.5 Oversampling Converters | 595 |
| Problems | 603 |
| References | 606 |
| | |
| 13 Nonlinear Amplifiers and Phase-Locked Loops | 607 |
| 13.1 Log/Antilog Amplifiers | 608 |
| 13.2 Analog Multipliers | 615 |
| 13.3 Operational Transconductance Amplifiers | 620 |
| 13.4 Phase-Locked Loops | 627 |
| 13.5 Monolithic PLLS | 635 |
| Problems | 642 |
| References | 646 |
| | |
| Index | 647 |